

University of Engineering and Technology, Taxila

Department of Computer Engineering



Lab Report 03

For the Course of DSD lab

Submitted By: Muhammad Ibrahim (21-CP-26)

Section: Omega

Lab Instructor: Sir Shahid Ali

Course Instructor: Dr. Abdul rehman aslam

Date: 26-01-24.

Course Title: DSD Lab

Lab Tasks

Question:

Task 1:


Design a full adder using two half adders using hierarchical modeling and other primitive logic gate (if required). Simulate and verify the following truth table in Xilinx ISE simulator.

Full Adder –Truth Table				
Input			Output	
A	B	Carry in	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

.....


A	B	C	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Half adder

 

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Full adder

 

A	B	Cin	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

```
//21_cp-26
module Task1(output S,Cout,input A,B,Cin);
wire w1,w2,w3;

half_adder ha1(.S(w1),.Cout(w2),.A(A),.B(B));
half_adder ha2(.S(S),.Cout(w3),.A(Cin),.B(w1));

or o1 (Cout,w2,w3);

endmodule

module half_adder(output S,Cout,input A,B);

xor x1(S,A,B);
and a1(Cout,A,B);

endmodule
```

//21_cp-26

```
module Task1(output S,Cout,input A,B,Cin);
wire w1,w2,w3;

half_adder ha1(.S(w1),.Cout(w2),.A(A),.B(B));
half_adder ha2(.S(S),.Cout(w3),.A(Cin),.B(w1));

or o1 (Cout,w2,w3);

endmodule

module half_adder(output S,Cout,input A,B);

xor x1(S,A,B);
and a1(Cout,A,B);

endmodule
```

TestBench:

```
module Task1tb;

    // Inputs
    reg A;
    reg B;
    reg Cin;

    // Outputs
    wire S;
    wire Cout;

    // Instantiate the Unit Under Test (UUT)
    Task1 uut (
        .S(S),
        .Cout(Cout),
        .A(A),
        .B(B),
        .Cin(Cin)
    );

    initial begin
        // Initialize Inputs
        A = 0;
        B = 0;
        Cin = 0;

        // Wait 100 ns for global reset to finish
        #100;
        #10 A=0;B=0;Cin=0;
        #10 A=0;B=0;Cin=1;
        #10 A=0;B=1;Cin=0;
        #10 A=0;B=1;Cin=1;
        #10 A=1;B=0;Cin=0;
        #10 A=1;B=0;Cin=1;
        #10 A=1;B=1;Cin=0;
        #10 A=1;B=1;Cin=1;

        // Add stimulus here

    end
endmodule
```

//21-CP-26

```
module Task1tb;
```

```
    // Inputs
```

```
    reg A;
```

```
    reg B;
```

```
    reg Cin;
```

```
    // Outputs
```

```
    wire S;
```

```
    wire Cout;
```

```
    // Instantiate the Unit Under Test (UUT)
```

```
    Task1 uut (
```

```

        .S(S),
        .Cout(Cout),
        .A(A),
        .B(B),
        .Cin(Cin)
    );

    initial begin
        // Initialize Inputs
        A = 0;
        B = 0;
        Cin = 0;

        // Wait 100 nfor global reset to finish
        #100;
        #10 A=0;B=0;Cin=0;
        #10 A=0;B=0;Cin=1;
        #10 A=0;B=1;Cin=0;
        #10 A=0;B=1;Cin=1;
        #10 A=1;B=0;Cin=0;
        #10 A=1;B=0;Cin=1;
        #10 A=1;B=1;Cin=0;
        #10 A=1;B=1;Cin=1;

        // Add stimulus here

    end



endmodule




```


Simulations :

As you can see the truth table verifies

Full Adder – Truth Table				
Input			Output	
A	B	Carry in	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 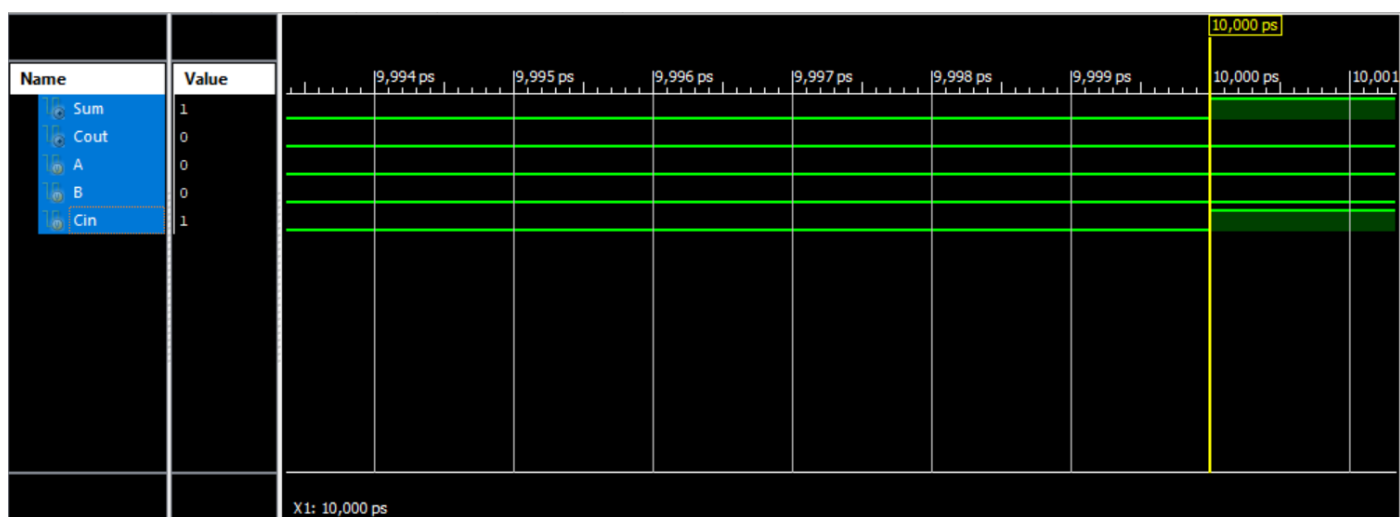

   

 

Question:




Task 2:

Design and stimulate 32-bit adder using a one-bit full adder. Show complete working of your solution. (Hint: Design an 8-bit adder using one-bit full adder, then instantiate these 8-bit adders to design a 32-bit adder).

Code:

Task 2 32 bit adder

One bit

   

A	B	Cin	Car	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0

```

module Task2(
output[31:0] S,
output Cout,
input [31:0]A,
input [31:0]B,
input Cin);
eight_bit_full_adder e1(.S(S[7:0]), .Cout(w8),.A(A[7:0]),.B(B[7:0]),.Cin(Cin));
eight_bit_full_adder e2(.S(S[15:8]), .Cout(w9),.A(A[15:8]),.B(B[15:8]),.Cin(w8));
eight_bit_full_adder e3(.S(S[23:16]), .Cout(w10),.A(A[23:16]),.B(B[23:16]),.Cin(w9));
eight_bit_full_adder e4(.S(S[31:24]), .Cout(w11),.A(A[31:24]),.B(B[31:24]),.Cin(w10));
or o1 (Cout,w8,w9,w10,w11);
endmodule

module eight_bit_full_adder(
output[7:0] S,
output Cout,
input [7:0]A,
input [7:0]B,
input Cin);
wire w1,w2,w3,w4,w5,w6,w7,w8;
one_bit_full_adder q1(.S(S[0]),.Cout(w1),.A(A[0]),.B(B[0]),.Cin(Cin));
one_bit_full_adder q2(.S(S[1]),.Cout(w2),.A(A[1]),.B(B[1]),.Cin(w1));
one_bit_full_adder q3(.S(S[2]),.Cout(w3),.A(A[2]),.B(B[2]),.Cin(w2));
one_bit_full_adder q4(.S(S[3]),.Cout(w4),.A(A[3]),.B(B[3]),.Cin(w3));
one_bit_full_adder q5(.S(S[4]),.Cout(w5),.A(A[4]),.B(B[4]),.Cin(w4));
one_bit_full_adder q6(.S(S[5]),.Cout(w6),.A(A[5]),.B(B[5]),.Cin(w5));
one_bit_full_adder q7(.S(S[6]),.Cout(w7),.A(A[6]),.B(B[6]),.Cin(w6));
one_bit_full_adder q8(.S(S[7]),.Cout(Cout),.A(A[7]),.B(B[7]),.Cin(w7));
endmodule

module one_bit_full_adder(output S,Cout,input A,B,Cin);
wire w1,w2,w3;
xor x1(w1,A,B);
xor x2(S,w1,Cin);
and a1(w2,w1,Cin);
and a2(w3,A,B);

xor x2(S,w1,Cin);
and a1(w2,w1,Cin);
and a2(w3,A,B);
or o1 (Cout,w2,w3);
endmodule

module half_adder(output S,Cout,input A,B);
xor x1(S,A,B);
and a1(Cout,A,B);
endmodule

```

```

module Task2(
output[31:0] S,
output Cout,
input [31:0]A,
input [31:0]B,
input Cin);
eight_bit_full_adder e1(.S(S[7:0]), .Cout(w8),.A(A[7:0]),.B(B[7:0]),.Cin(Cin));
eight_bit_full_adder e2(.S(S[15:8]), .Cout(w9),.A(A[15:8]),.B(B[15:8]),.Cin(w8));
eight_bit_full_adder e3(.S(S[23:16]), .Cout(w10),.A(A[23:16]),.B(B[23:16]),.Cin(w9));
eight_bit_full_adder e4(.S(S[31:24]), .Cout(w11),.A(A[31:24]),.B(B[31:24]),.Cin(w10));
or o1 (Cout,w8,w9,w10,w11);
endmodule

```

```

module eight_bit_full_adder(
output[7:0] S,
output Cout,
input [7:0]A,
input [7:0]B,
input Cin);
wire w1,w2,w3,w4,w5,w6,w7,w8;
one_bit_full_adder q1(.S(S[0]),.Cout(w1),.A(A[0]),.B(B[0]),.Cin(Cin));
one_bit_full_adder q2(.S(S[1]),.Cout(w2),.A(A[1]),.B(B[1]),.Cin(w1));
one_bit_full_adder q3(.S(S[2]),.Cout(w3),.A(A[2]),.B(B[2]),.Cin(w2));
one_bit_full_adder q4(.S(S[3]),.Cout(w4),.A(A[3]),.B(B[3]),.Cin(w3));
one_bit_full_adder q5(.S(S[4]),.Cout(w5),.A(A[4]),.B(B[4]),.Cin(w4));
one_bit_full_adder q6(.S(S[5]),.Cout(w6),.A(A[5]),.B(B[5]),.Cin(w5));
one_bit_full_adder q7(.S(S[6]),.Cout(w7),.A(A[6]),.B(B[6]),.Cin(w6));
one_bit_full_adder q8(.S(S[7]),.Cout(Cout),.A(A[7]),.B(B[7]),.Cin(w7));
endmodule

```

```

module one_bit_full_adder(output S,Cout,input A,B,Cin);
wire w1,w2,w3;
xor x1(w1,A,B);
xor x2(S,w1,Cin);
and a1(w2,w1,Cin);
and a2(w3,A,B);
or o1(Cout,w2,w3);
endmodule

```

```

module half_adder(output S,Cout,input A,B);
xor x1(S,A,B);
and a1(Cout,A,B);
endmodule

```

TestBench:

```

module Task2tb;

// Inputs
reg [31:0] A;
reg [31:0] B;
reg Cin;

// Outputs
wire [31:0] S;
wire Cout;

// Instantiate the U
Task2 uut: {
    .S(S),
    .Cout(Cout),
    .A(A),
    .B(B),
    .Cin(Cin)
};

initial begin
    // Initialize Inputs
    A = 0;
    B = 0;
    Cin = 0;

    // Wait 100 ns for global reset to finish
    #100;
    A = 32'h11111111111111111111111111111111;
    B = 32'h00000000000000000000000000000010;
    #10
    A = 32'h11111111111111111111111111111111;
    B = 32'h11111000000000000000000000000010;

end
endmodule

```

```

1 //21-cp-26
2 module t2tb;
3 // Inputs
4 reg [31:0] A;
5 reg [31:0] B;
6 reg Cin;
7 // Outputs
8 wire [31:0] Sum;
9 wire [31:0] Cout;
10 // Instantiate the Unit Under Test: (UUT)
11 t2 uut: {
12     .A(A),
13     .B(B),
14     .Cin(Cin),
15     .Sum(Sum),
16     .Cout(Cout)
17 };
18 initial begin
19     // Initialize Inputs
20     A = 0;
21     B = 0;
22     Cin = 0;
23     // Wait 100 ns for global reset to finish
24     #10; A = 32'h11001100110011001100110011001100;
25     B = 32'h00110011001100110011001100110011;
26     Cin = 1;
27     #10 A = 32'h11001100110011001100110011001100;
28     B = 32'h00110011001100110011001100110011;
29     #10 A = 32'h11111111111111111111111111111111;
30     B = 32'h00000000000000000000000000000001;
31
32     A = 32'h11111111111111111111111111111111;
33     B = 32'h00000000000000000000000000000001;
34
35     A = 32'h11001100110011001100110011001100;
36     B = 32'h00110011001100110011001100110011;
37     A = 32'h11001100110011001100110011001100;
38     B = 32'h00110011001100110011001100110011;
39     Cin = 1;
40     #10
41     A = 32'h11001100110011001100110011001100;
42     B = 32'h00110011001100110011001100110011;
43     #10 A = 32'h11111111111111111111111111111111;
44     B = 32'h00000000000000000000000000000001;
45     Cin=0;
46     end
47
48 endmodule
49

```

//

//21-cp-26

```

module t2tb;

// Inputs
    reg [31:0] A;
    reg [31:0] B;
    reg Cin;

// Outputs
    wire [31:0] Sum;
    wire [31:0] Cout;

    // Instantiate the Unit Under Test (UUT)
    t2 uut (
        .A(A),
        .B(B),
        .Cin(Cin),
        .Sum(Sum),
        .Cout(Cout)
    );

initial begin

// Initialize Inputs
    A = 0;
    B = 0;
    Cin = 0;

// Wait 100 ns for global reset to finish
#10; A = 32'b11001100110011001100110011001100;
    B = 32'b00110011001100110011001100110011;
    Cin = 1;

#10      A = 32'b11001100110011001100110011001100;
    B = 32'b00110011001100110011001100110011;

#10 A = 32'b11111111111111111111111111111111;
    B = 32'b00000000000000000000000000000001;

A = 32'b11111111111111111111111111111111;
B = 32'b00000000000000000000000000000001;

A = 32'b11001100110011001100110011001100;
B = 32'b00110011001100110011001100110011;

```



```
A = 32'b11001100110011001100110011001100;  
B = 32'b00110011001100110011001100110011;  
Cin = 1;
```




#10

```
    A = 32'b11001100110011001100110011001100;  
    B = 32'b00110011001100110011001100110011;  
#10 A = 32'b11111111111111111111111111111111;  
B = 32'b00000000000000000000000000000001;  
Cin=0;  
    end
```

endmodule

Simulations :

  

 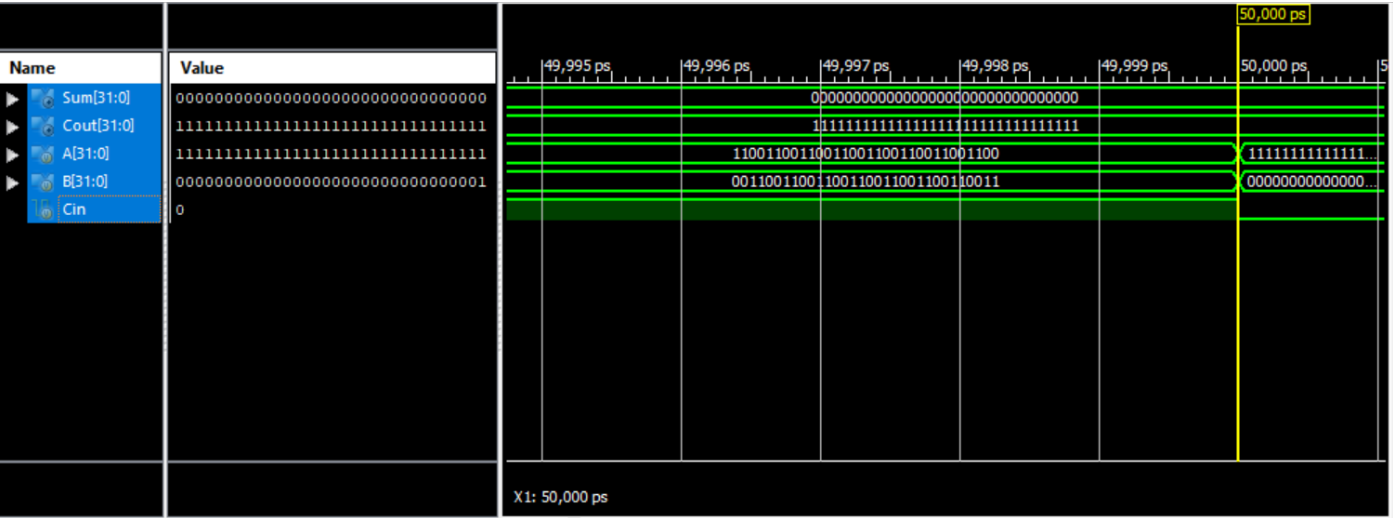 

Question:

Task 3:

Design and simulate a BCD to Seven Segment Converter Using 2-to-1 Multiplexers Only. You cannot use any other component or primitive gate. Show complete working of your solution.

Code:

```
module Task3(  
    input [3:0] x,  
    output a  
);  
wire w0,w1,w2,w3,w4,w5,w6,w7,w8,w9;  
not n1(w0,x[2]);  
not n2(w1,x[0]);  
not n3(w9,x[1]);  
and a1(w2,w0,w1);  
and a2(w3,x[2],x[0]);  
or o1(w4,w2,w3,x[1]);  
and a3(w5,x[2],x[1]);  
and a4(w7,w9,w0);  
or O2(w8,w5,w7,w1);  
mux_2 m1(.a(w4),.b(w8),.s(x[3]),.f(a));  
endmodule  
  
module mux_2(  
    input a,  
    input b,  
    input s,  
    output f  
);  
wire w1,w2,w3,w4;  
and a1(w1,a,b);  
and a2(w2,s,b);  
not n1(w3,s);  
and a3(w4,w3,a);  
or o1(f,w1,w2,w4);  
endmodule
```

```
module Task3(  
    input [3:0] x,  
    output a  
);  
wire w0,w1,w2,w3,w4,w5,w6,w7,w8,w9;  
not n1(w0,x[2]);  
not n2(w1,x[0]);  
not n3(w9,x[1]);  
and a1(w2,w0,w1);  
and a2(w3,x[2],x[0]);  
or o1(w4,w2,w3,x[1]);  
and a3(w5,x[2],x[1]);  
and a4(w7,w9,w0);  
or O2(w8,w5,w7,w1);
```

```
mux_2 m1(.a(w4),.b(w8),.s(x[3]),.f(a));  
endmodule
```

```
module mux_2(  
    input a,  
    input b,  
    input s,  
    output f  
);  
wire w1,w2,w3,w4;  
and a1(w1,a,b);  
and a2(w2,s,b);  
not n1(w3,s);  
and a3(w4,w3,a);  
or o1(f,w1,w2,w4);  
endmodule
```

TestBench:

```

module Task3tb;

    reg [3:0] x;

    // Outputs
    wire a;

    // Instantiate the Unit Under Test (UUT)
    Task3 uut (
        .x(x),
        .a(a)
    );

    initial begin
x = 0;
        #100;
        x = 1;
        #100;
        x = 2;
        #100;
        x = 3;
        #100;
        x = 4;
        #100;
        x = 5;
        #100;
        x = 6;
        #100;
        x = 7;
        #100;
        x = 8;
        #100;
        x = 9;
        #100;
        x =1010;
        #100;
        x =1011;
        #100;
        x =1100;
        #100;
        x =1101 ;
        #100;
        x =1110;
        #100;
        x =1111;
    end

```

```
module Task3tb;
```

```
    reg [3:0] x;
```

```
    // Outputs
```

```
    wire a;
```

```
    // Instantiate the Unit Under Test (UUT)
```

```
    Task3 uut (
```

```
        .x(x),
```

```
        .a(a)
```

);

initial begin

x = 0;

#100;

x = 1;

#100;

x = 2;

#100;

x = 3;

#100;

x = 4;

#100;

x = 5;

#100;

x = 6;

#100;

x = 7;

#100;

x = 8;

#100;

x = 9;

#100;

x =1010;

#100;

x =1011;

#100;

x =1100;

#100;

x =1101 ;

#100;

x =1110;

#100;

x =1111;

end

endmodule

Simulations :

