

University of Engineering and Technology, Taxila

Department of Computer Engineering



Lab Report 04

For the Course of DSD lab

Submitted By: Muhammad Ibrahim (21-CP-26)

Section: Omega

Lab Instructor: Sir Shahid Ali

Course Instructor: Dr. Abdul rehman aslam

Date: 11-02-24.


Course Title: DSD Lab

Question 1:

5 Lab Tasks: You can use only Data-Flow Modeling in this Lab.

 1. Simulate 2×4 decoder, given in the following diagram, using **assign** statement only.


- Neglect the propagation delays, simulate the design, and analyse the output. Are all the outputs in all three parts the same or different?
- Consider propagation delay of inverter **N1** is **5 time-units** and propagation delay of the and gate **A1** is **6 time-units** and change input values in testbench after each **5 timeunits**. Analyze the output.
- Now change the propagation delay of **A1** to **5 time-units** as well and keep changing the input values in testbench after each **5 time-units**. Analyze the output again.



Task


2x4 decoder

Using assign statement

 

$n = 2n$



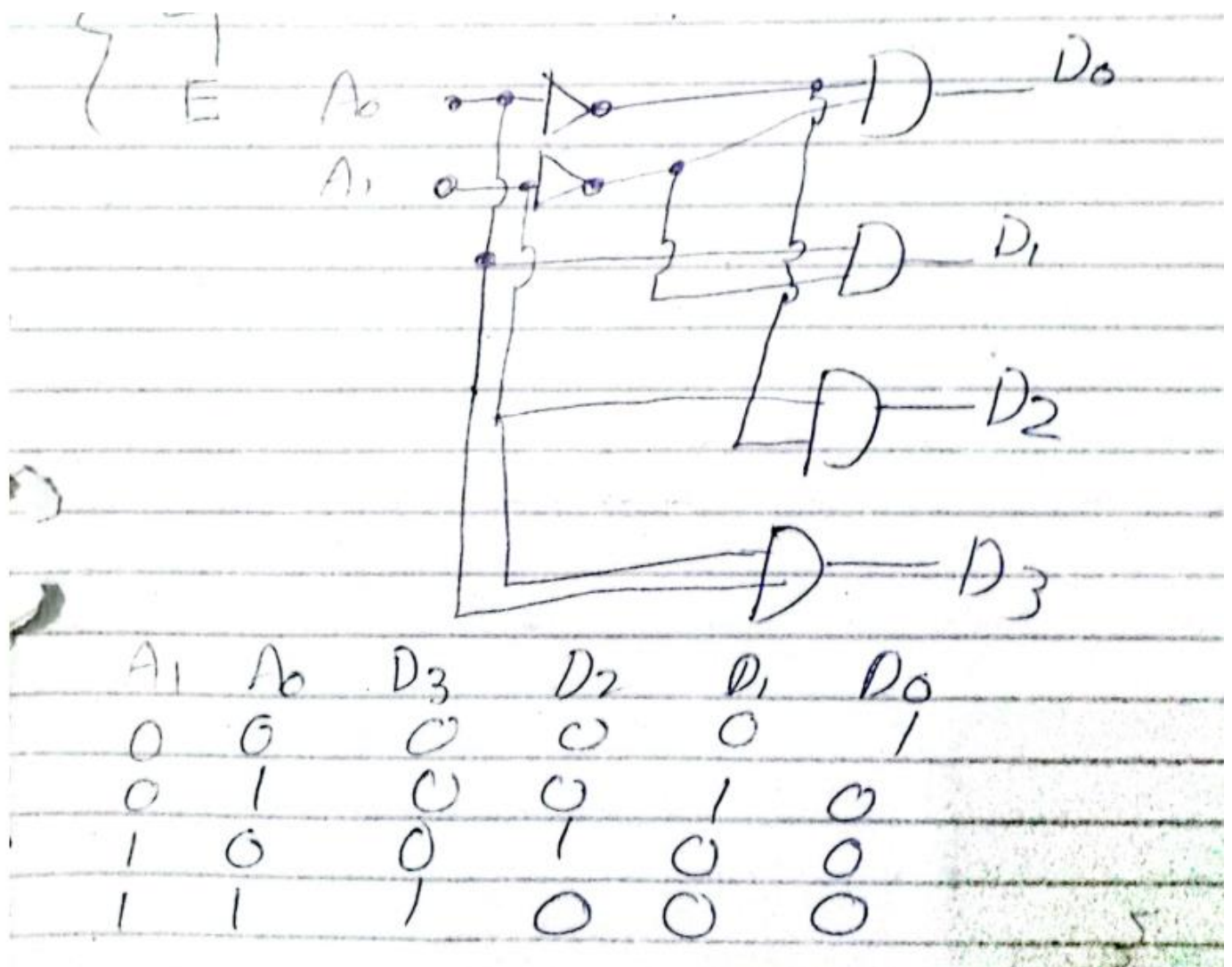

Code:

```

module Task1(output [3:0] G, input A0, A1);
    wire w1, w2, w3, w4;

    not_gate n1 (.A(w1), .B(A0));
    not_gate n2 (.A(w2), .B(A1));
    and_gate a1 (.Y(G[0]), .X(w1), .Z(w2));
    and_gate a2 (.Y(G[1]), .X(A0), .Z(w2));
    and_gate a3 (.Y(G[2]), .X(A1), .Z(w1));
    and_gate a4 (.Y(G[3]), .X(A0), .Z(A1));
endmodule

module and_gate(output Y, input X, Z);
    assign Y = X & Z;
endmodule

module not_gate(output A, input B);
    assign A = !B;
endmodule

```

```
module Task1(output [3:0] G, input A0, A1);
```

```
    wire w1, w2, w3, w4;
```

```
    not_gate n1 (.A(w1), .B(A0));
```

```
    not_gate n2 (.A(w2), .B(A1));
```

```
    and_gate a1 (.Y(G[0]), .X(w1), .Z(w2));
```

```
    and_gate a2 (.Y(G[1]), .X(A0), .Z(w2));
```

```
    and_gate a3 (.Y(G[2]), .X(A1), .Z(w1));
```

```
    and_gate a4 (.Y(G[3]), .X(A0), .Z(A1));
```

```
endmodule
```

```
module and_gate(output Y, input X, Z);
```

```
    assign Y = X & Z;
```

```
endmodule
```

```
module not_gate(output A, input B);
```

```
    assign A = !B;
```

```
endmodule
```

TestBench:

A ₁	A ₀	D ₃	D ₂	D ₁	D ₀
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

```

module Task1Tb;

    // Inputs
    reg A0;
    reg A1;

    // Outputs
    wire [3:0] G;

    // Instantiate the Unit Under Test (UUT)
    Task1 uut (
        .G(G),
        .A0(A0),
        .A1(A1)
    );

    initial begin
        // Initialize Inputs
        A0 = 0;
        A1 = 0;

        // Wait 100 ns for global reset to finish
        #100;
        A0 = 0;
        A1 = 0;
        #10
        A0 = 0;
        A1 = 1;
        #10
        A0 = 1;
        A1 = 0;
        #10
        A0 = 1;
        A1 = 1;

        // Add stimulus here

    end
endmodule

```

```

module Task1Tb;

```

```

    // Inputs

```

```

    reg A0;

```

```

    reg A1;

```

```

    // Outputs

```

```

    wire [3:0] G;

```

```

    // Instantiate the Unit Under Test (UUT)

```

```

    Task1 uut (

```

```

        .G(G),

```

```

        .A0(A0),

```

```

        .A1(A1)

```

```

    );

```

```

    initial begin




```


```
// Initialize Inputs  
  
A0 = 0;  
A1 = 0;  
  
// Wait 100 ns for global reset to finish  
  
#100;  
  
A0 = 0;  
A1 = 0;  
  
#10  
  
A0 = 0;  
A1 = 1;  
  
#10  
  
A0 = 1;  
A1 = 0;  
  
#10  
  
A0 = 1;  
A1 = 1;  
  
// Add stimulus here
```

```
end
```

```
endmodule
```

Simulations :

   

 

Part B:

- b) Consider propagation delay of inverter **N1** is **5 time-units** and propagation delay of the and gate **A1** is **6 time-units** and change input values in testbench after each **5 timeunits**. Analyze the output.

Code:

```
module Task1b(output [3:0] G, input A0, A1);
    wire w1, w2, w3, w4;
    assign #5 w1=!A1;
    not_gate1 n2 (.A(w2), .B(A1));
    assign #6 G[0]=w1&w2;
    and_gate1 a2 (.Y(G[1]), .X(A0), .Z(w2));
    and_gate1 a3 (.Y(G[2]), .X(A1), .Z(w1));
    and_gate1 a4 (.Y(G[3]), .X(A0), .Z(A1));
endmodule

module and_gate1(output Y, input X, Z);
    assign Y = X & Z;
endmodule

module not_gate1(output A, input B);
    assign A = !B;
endmodule
```

```
module Task1b(output [3:0] G, input A0, A1);
```

```
    wire w1, w2, w3, w4;
```

```
    assign #5 w1=!A1;
```

```
    not_gate1 n2 (.A(w2), .B(A1));
```



```

assign #6 G[0]=w1&w2;

and_gate1 a2 (.Y(G[1]), .X(A0), .Z(w2));

and_gate1 a3 (.Y(G[2]), .X(A1), .Z(w1));

and_gate1 a4 (.Y(G[3]), .X(A0), .Z(A1));

endmodule

```

```

module and_gate1(output Y, input X, Z);

    assign Y = X & Z;

endmodule

```

```

module not_gate1(output A, input B);

    assign A = !B;

endmodule

```

TestBench:

A ₁	A ₀	D ₃	D ₂	D ₁	D ₀
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

```

module Task1bTb;

    // Inputs
    reg A0;
    reg A1;

    // Outputs
    wire [3:0] G;

    // Instantiate the Unit Under Test (UUT)
    Task1b uut (
        .G(G),
        .A0(A0),
        .A1(A1)
    );

    initial begin
        // Initialize Inputs
        A0 = 0;
        A1 = 0;

        // Wait 100 ns for global reset to finish
        #100;

        #5
        A0 = 0;
        A1 = 1;
        #5
        A0 = 1;
        A1 = 0;
        #5
        A0 = 0;
        A1 = 1;

        // Add stimulus here

```

```

module Task1bTb;

```

```

    // Inputs

```

```

    reg A0;

```

```

    reg A1;

```

```

    // Outputs

```

```

    wire [3:0] G;

```

```

    // Instantiate the Unit Under Test (UUT)

```

```

    Task1b uut (

```

```

        .G(G),

```

```

        .A0(A0),

```

```

        .A1(A1)

```

);

initial begin

 // Initialize Inputs

 A0 = 0;

 A1 = 0;

 // Wait 100 ns for global reset to finish

 #100;

 #5

 A0 = 0;

 A1 = 1;

 #5

 A0 = 1;

 A1 = 0;

 #5

 A0 = 0;




 A1 = 1;



 // Add stimulus here

end

endmodule

Simulations :

   

  

Part C:

- c) Now change the propagation delay of **A1** to **5 time-units** as well and keep changing the input values in testbench after each **5 time-units**. Analyze the output again.

Code:

```
module Task1C(output [3:0] G, input A0, A1);
    wire w1, w2, w3, w4;

    not_gate2 n1 (.A(w1), .B(A0));
    not_gate2 n2 (.A(w2), .B(A1));
    assign #5 G[0]=w1&w2;
    and_gate2 a2 (.Y(G[1]), .X(A0), .Z(w2));
    and_gate2 a3 (.Y(G[2]), .X(A1), .Z(w1));
    and_gate2 a4 (.Y(G[3]), .X(A0), .Z(A1));
endmodule

module and_gate2(output Y, input X, Z);
    assign Y = X & Z;
endmodule

module not_gate2(output A, input B);
    assign A = !B;
endmodule
```

```
module Task1C(output [3:0] G, input A0, A1);
```

```
    wire w1, w2, w3, w4;
```

```
    not_gate2 n1 (.A(w1), .B(A0));
```

```
    not_gate2 n2 (.A(w2), .B(A1));
```

```
    assign #5 G[0]=w1&w2;
```

```
    and_gate2 a2 (.Y(G[1]), .X(A0), .Z(w2));
```

```
    and_gate2 a3 (.Y(G[2]), .X(A1), .Z(w1));
```

```
    and_gate2 a4 (.Y(G[3]), .X(A0), .Z(A1));
```

```
endmodule
```

```

module and_gate2(output Y, input X, Z);

    assign Y = X & Z;

endmodule

```

```

module not_gate2(output A, input B);

    assign A = !B;

endmodule

```

TestBench:

A ₁	A ₀	D ₃	D ₂	D ₁	D ₀
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

```

module Task1CTb;

    reg A0;
    reg A1;

    // Outputs
    wire [3:0] G;

    // Instantiate the Unit Under Test (UUT)
    Task1C uut (
        .G(G),
        .A0(A0),
        .A1(A1)
    );

    initial begin
        // Initialize Inputs
        A0 = 0;
        A1 = 0;

        // Wait 100 ns for global reset to finish
        #100;
        A0 = 0;
        A1 = 1;
        A0 = 1;
        A1 = 0;
        A0 = 1;
        A1 = 1;

        // Add stimulus here

    end

endmodule

```

```

module Task1CTb;

```

```
reg A0;
```

```
reg A1;
```

```
// Outputs
```

```
wire [3:0] G;
```

```
// Instantiate the Unit Under Test (UUT)
```

```
Task1C uut (
```

```
    .G(G),
```

```
    .A0(A0),
```

```
    .A1(A1)
```

```
);
```

```
initial begin
```

```
    // Initialize Inputs
```

```
    A0 = 0;
```

```
    A1 = 0;
```

```
    // Wait 100 ns for global reset to finish
```

```
    #100;
```

```
    A0 = 0;
```

```
    A1 = 1;
```

```
    A0 = 1;
```

```
    A1 = 0;
```

```
    A0 = 1;
```


```
    A1 = 1;
```


```
    // Add stimulus here
```

```
end
```

```
endmodule
```






Simulations :

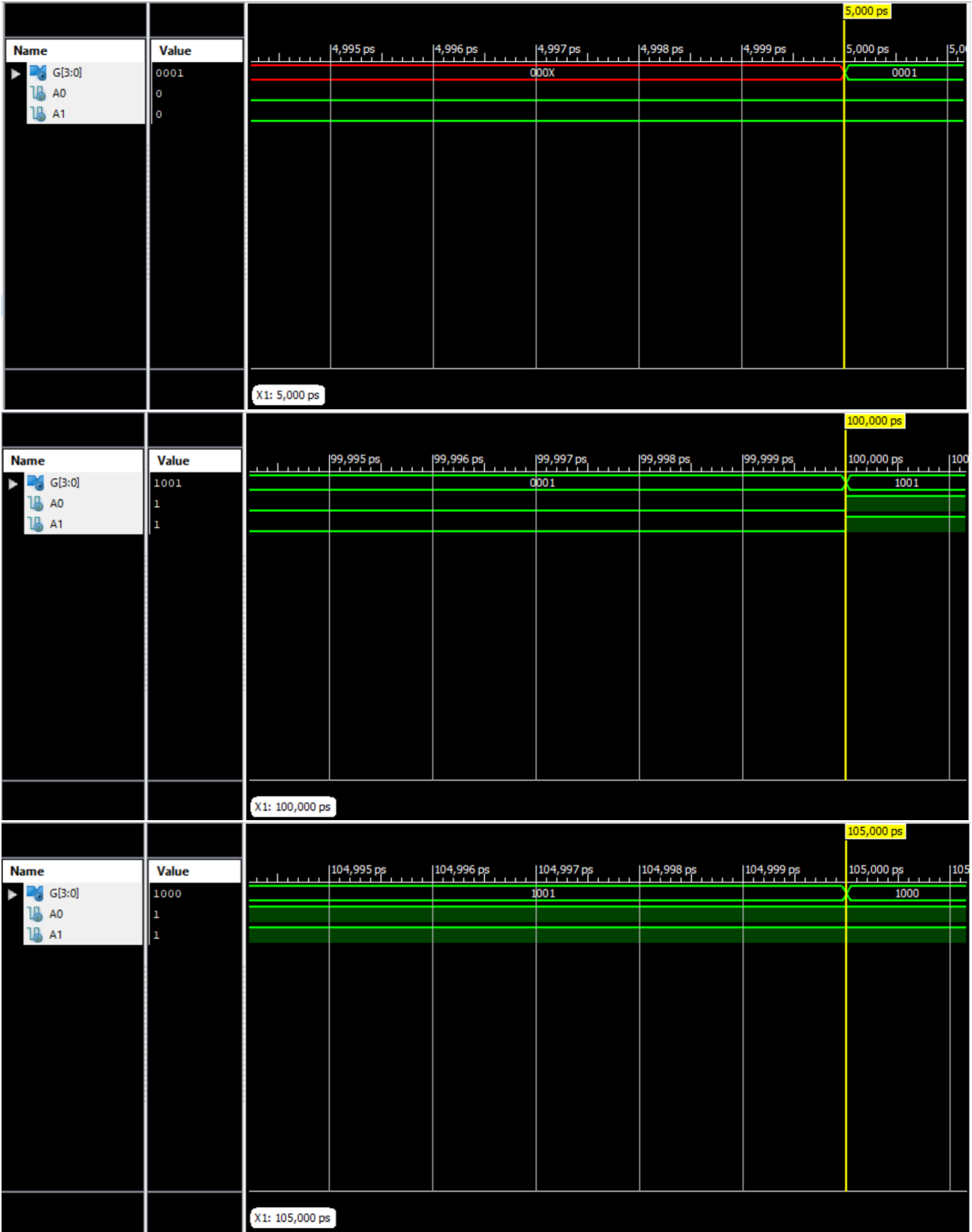

     


Question No 2:

- Design and simulate 8×1 MUX using conditional operator in data-flow modeling. Show circuit diagram and truth table as well.



INPUTS			Output
S_2	S_1	S_0	Y
0	0	0	A_0
0	0	1	A_1
0	1	0	A_2
0	1	1	A_3
1	0	0	A_4
1	0	1	A_5
1	1	0	A_6
1	1	1	A_7

 

Code:

```

module m2x1_mux(output Y,input A0,A1,input S0);
wire w1,w2,w3;
assign Y=S0?A1:A0;

endmodule

module m4x1_mux(output Y,input A0,A1,A2,A3,input S0,S1);
wire w4,w5;
m2x1_mux m1(.Y(w4),.A0(A0),.A1(A1),.S0(S0));
m2x1_mux m2(.Y(w5),.A0(A2),.A1(A3),.S0(S0));
m2x1_mux m3(.Y(Y),.A0(w4),.A1(w5),.S0(S1));

endmodule

module Task2(output Y,input A0,A1,A2,A3,A4,A5,A6,A7,input S0,S1,S2,S3);
wire w6,w7;
m4x1_mux M4(.Y(w6),.A0(A0),.A1(A1),.A2(A2),.A3(A3),.S0(S0),.S1(S1));
m4x1_mux M5(.Y(w7),.A0(A4),.A1(A5),.A2(A6),.A3(A7),.S0(S0),.S1(S1));
m2x1_mux m6(.Y(Y),.A0(w6),.A1(w7),.S0(S2));

endmodule

```

```
module m2x1_mux(output Y,input A0,A1,input S0);
```

```
wire w1,w2,w3;
```

```
assign Y=S0?A1:A0;
```

```
endmodule
```

```
module m4x1_mux(output Y,input A0,A1,A2,A3,input S0,S1);
```

```
wire w4,w5;
```

```
m2x1_mux m1(.Y(w4),.A0(A0),.A1(A1),.S0(S0));
```

```
m2x1_mux m2(.Y(w5),.A0(A2),.A1(A3),.S0(S0));
```

```
m2x1_mux m3(.Y(Y),.A0(w4),.A1(w5),.S0(S1));
```

```
endmodule
```

```
module Task2(output Y,input A0,A1,A2,A3,A4,A5,A6,A7,input S0,S1,S2,S3);
```

```
wire w6,w7;
```

```
m4x1_mux M4(.Y(w6),.A0(A0),.A1(A1),.A2(A2),.A3(A3),.S0(S0),.S1(S1));
```

```
m4x1_mux M5(.Y(w7),.A0(A4),.A1(A5),.A2(A6),.A3(A7),.S0(S0),.S1(S1));
```

```
m2x1_mux m6(.Y(Y),.A0(w6),.A1(w7),.S0(S2));
```

endmodule

TestBench:

```
module Task2Tb;

    // TopGate
    reg A0;
    reg A1;
    reg A2;
    reg A3;
    reg A4;
    reg A5;
    reg A6;
    reg A7;
    reg Z0;
    reg Z1;
    reg Z2;
    reg Z3;

    // Output
    wire Y;

    // Instantiate the DUT Under Test (DUT)
    Task2 uut (
        .Y(Y),
        .A0(A0),
        .A1(A1),
        .A2(A2),
        .A3(A3),
        .A4(A4),
        .A5(A5),
        .A6(A6),
        .A7(A7),
        .Z0(Z0),
        .Z1(Z1),
        .Z2(Z2),
        .Z3(Z3)
    );

    // Initial Inputs
    // Initialize TopGate
    A0 = 0;
    A1 = 0;
    A2 = 0;
    A3 = 0;
    A4 = 0;
    A5 = 0;
    A6 = 0;
    A7 = 0;
    Z0 = 0;
    Z1 = 0;
    Z2 = 0;
    Z3 = 0;

    // Wait 100 ns for global reset to finish
    #100;

    A0 = 0; A1 = 0; A2 = 0; A3 = 0; A4 = 0; A5 = 0; A6 = 0; A7 = 0; Z0 = 0; Z1 = 0; Z2 = 0; Z3 = 0;

    // Add activation here
    A0 = 0; A1 = 0; A2 = 0; A3 = 0; A4 = 0; A5 = 0; A6 = 0; A7 = 1; Z0 = 0; Z1 = 0; Z2 = 0; Z3 = 1;
    A0 = 0; A1 = 0; A2 = 0; A3 = 0; A4 = 0; A5 = 0; A6 = 1; A7 = 0; Z0 = 0; Z1 = 0; Z2 = 1; Z3 = 0;
    A0 = 0; A1 = 0; A2 = 0; A3 = 0; A4 = 0; A5 = 0; A6 = 1; A7 = 1; Z0 = 0; Z1 = 0; Z2 = 1; Z3 = 1;
    A0 = 0; A1 = 0; A2 = 0; A3 = 0; A4 = 0; A5 = 1; A6 = 0; A7 = 0; Z0 = 0; Z1 = 1; Z2 = 0; Z3 = 0;
    A0 = 0; A1 = 0; A2 = 0; A3 = 0; A4 = 0; A5 = 1; A6 = 0; A7 = 1; Z0 = 0; Z1 = 1; Z2 = 0; Z3 = 1;
    A0 = 0; A1 = 0; A2 = 0; A3 = 0; A4 = 0; A5 = 1; A6 = 1; A7 = 0; Z0 = 0; Z1 = 1; Z2 = 1; Z3 = 0;
    A0 = 0; A1 = 0; A2 = 0; A3 = 0; A4 = 0; A5 = 1; A6 = 1; A7 = 1; Z0 = 0; Z1 = 1; Z2 = 1; Z3 = 1;
    A0 = 0; A1 = 0; A2 = 0; A3 = 0; A4 = 0; A5 = 0; A6 = 0; A7 = 0; Z0 = 0; Z1 = 0; Z2 = 0; Z3 = 0;

    // Add activation here
    A0 = 0; A1 = 0; A2 = 0; A3 = 0; A4 = 0; A5 = 1; A6 = 1; A7 = 1; Z0 = 0; Z1 = 1; Z2 = 1; Z3 = 1;
    A0 = 0; A1 = 0; A2 = 0; A3 = 0; A4 = 0; A5 = 0; A6 = 0; A7 = 0; Z0 = 0; Z1 = 0; Z2 = 0; Z3 = 0;

endmodule
```

module Task2Tb;

// Inputs

reg A0;

reg A1;

reg A2;

reg A3;

reg A4;

reg A5;

reg A6;

```
reg A7;
```

```
reg S0;
```

```
reg S1;
```

```
reg S2;
```

```
reg S3;
```

```
// Outputs
```

```
wire Y;
```

```
// Instantiate the Unit Under Test (UUT)
```

```
Task2 uut (
```

```
    .Y(Y),
```

```
    .A0(A0),
```

```
    .A1(A1),
```

```
    .A2(A2),
```

```
    .A3(A3),
```

```
    .A4(A4),
```

```
    .A5(A5),
```

```
    .A6(A6),
```

```
    .A7(A7),
```

```
    .S0(S0),
```

```
    .S1(S1),
```

```
    .S2(S2),
```

```
    .S3(S3)
```

```
);
```

```
initial begin
```

```
    // Initialize Inputs
```

```
    A0 = 0;
```

```
    A1 = 0;
```

```
    A2 = 0;
```

```
    A3 = 0;
```

```
    A4 = 0;
```

```
    A5 = 0;
```


A6 = 0;

A7 = 0;

S0 = 0;

S1 = 0;

S2 = 0;

S3 = 0;

// Wait 100 ns for global reset to finish

#100;

A0 = 0; A1 = 0; A2 = 0; A3 = 0; A4 = 0; A5 = 0; A6 = 0; A7 = 0; S0 = 0; S1 = 0; S2 = 0; S3 = 0;

// Add stimulus here

A0 = 0; A1 = 0; A2 = 0; A3 = 0; A4 = 0; A5 = 0; A6 = 0; A7 = 1; S0 = 0; S1 = 0; S2 = 0; S3 = 1;

A0 = 0; A1 = 0; A2 = 0; A3 = 0; A4 = 0; A5 = 0; A6 = 1; A7 = 0; S0 = 0; S1 = 0; S2 = 1; S3 = 0;

A0 = 0; A1 = 0; A2 = 0; A3 = 0; A4 = 0; A5 = 0; A6 = 1; A7 = 1; S0 = 0; S1 = 0; S2 = 1; S3 = 1;

A0 = 0; A1 = 0; A2 = 0; A3 = 0; A4 = 0; A5 = 1; A6 = 0; A7 = 0; S0 = 0; S1 = 1; S2 = 0; S3 = 0;

A0 = 0; A1 = 0; A2 = 0; A3 = 0; A4 = 0; A5 = 1; A6 = 0; A7 = 1; S0 = 0; S1 = 1; S2 = 0; S3 = 1;

A0 = 0; A1 = 0; A2 = 0; A3 = 0; A4 = 0; A5 = 1; A6 = 1; A7 = 0; S0 = 0; S1 = 1; S2 = 1; S3 = 0;

// Add stimulus here

A0 = 0; A1 = 0; A2 = 0; A3 = 0; A4 = 0; A5 = 1; A6 = 1; A7 = 1; S0 = 0; S1 = 1; S2 = 1; S3 = 1;

A0 = 0; A1 = 0; A2 = 0; A3 = 0; A4 = 0; A5 = 0; A6 = 0; A7 = 0; S0 = 0; S1 = 0; S2 = 0; S3 = 0;

A0 = 0; A1 = 0; A2 = 0; A3 = 0; A4 = 1; A5 = 0; A6 = 0; A7 = 1; S0 = 1; S1 = 0; S2 = 0; S3 = 1;



A0 = 0; A1 = 0; A2 = 0; A3 = 0; A4 = 1; A5 = 0; A6 = 1; A7 = 0; S0 = 1; S1 = 0; S2 = 1; S3 = 0;

A0 = 0; A1 = 0; A2 = 0; A3 = 0; A4 = 1; A5 = 0; A6 = 1; A7 = 1; S0 = 1; S1 = 0; S2 = 1; S3 = 1;

end


endmodule

Simulations :

  

Question:

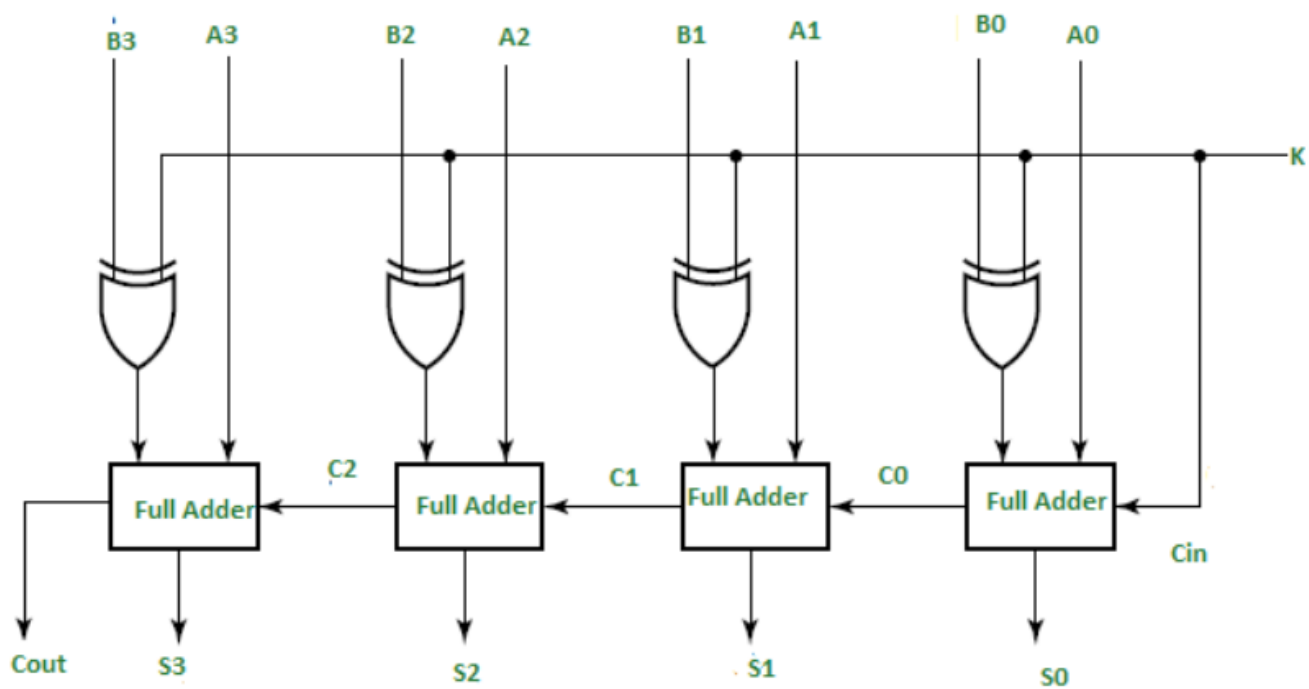3. Design and simulate 4-bit **Subtractor**. Show the block diagram and truth table as well.



Cin	A				B				Difference				Borrow
	A3	A2	A1	A0	B3	B2	B1	B0	d3	d2	d1	d0	Bout
0	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	1	0	0	0	0	0
0	0	0	1	0	0	0	1	0	0	0	0	0	0
0	0	0	1	1	0	0	1	1	0	0	0	0	0
0	0	1	0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0	1	0	0	0	0	0
0	0	1	1	0	0	1	1	0	0	0	0	0	0
0	0	1	1	1	0	1	1	1	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0	0	0	0
0	1	0	0	1	1	0	0	1	0	0	0	0	0
0	1	0	1	0	1	0	1	0	0	0	0	0	0
0	1	0	1	1	1	0	1	1	0	0	0	0	0
0	1	1	0	0	1	1	0	0	0	0	0	0	0
0	1	1	0	1	1	1	0	1	0	0	0	0	0
0	1	1	1	0	1	1	1	0	0	0	0	0	0
0	1	1	1	1	1	1	1	1	0	0	0	0	0

Code:

```

module Task3(
output [3:0] Y
,output Cout
,input[3:0] A
,input [3:0] B,
input Bin );
wire [3:0] W;
wire C0,C1,C2,C3;
wire X0,X1,X2,X3;

//xor
assign X3=B[3]^Bin;
assign X2=B[2]^Bin;
assign X1=B[1]^Bin;
assign X0=B[0]^Bin;


full_1_adder fa1(Y[0],C0,A[0],X0,Bin);
full_1_adder fa2(Y[1],C1,A[1],X1,C0);
full_1_adder fa3(Y[2],C2,A[2],X2,C1);
full_1_adder fa4(Y[3],Cout,A[3],X3,C2);


endmodule

module full_1_adder(output Y,Cout,input A,B,Cin);

assign w1=A^B;
assign Y=w1^Cin;
assign w2=w1&Cin;
assign w3=A&B;
assign Cout=w2+w3;


endmodule

```

TestBench:

```
module Task3Tb;
```

```
    // Inputs
```

```
    reg [3:0] A;
```

```
    reg [3:0] B;
```

```
    reg Bin;
```

```
    // Outputs
```

```
    wire [3:0] Y;
```

```
    wire Cout;
```

```
    // Instantiate the Unit Under Test (UUT)
```

```
    Task3 uut (
```

```
        .Y(Y),
```

```
        .Cout(Cout),
```

```
        .A(A),
```

```
        .B(B),
```

```
        .Bin(Bin)
```

```
    );
```

```
    initial begin
```

```
        // Initialize In
```

```
        A = 4'b0101;
```

```
        B = 4'b0011;
```

```
        Bin = 0;
```

```
        #100;
```

```
        #10    A = 0000;B = 0000;Bin = 1;
```

```
        #10    A = 00001;B = 0001;Bin = 0;
```

```
        #10    A = 0010;B = 0010;Bin = 1;
```

```
        #10    A = 0011;B = 0011;Bin = 0;
```

```
        #10    A = 0100;B = 0100;Bin = 1;
```

```
        #10    A = 0101;B = 0101;Bin = 0;
```

```
        #10    A = 0110;B = 0110;Bin = 1;
```

```
#10    A = 0111;B = 0111;Bin = 0;
```

```
#10    A = 1000;B = 1000;Bin = 1;
```

```
#10    A = 1001;B = 1001;Bin = 0;
```

```
#10    A = 1010;B = 1010;Bin = 1;
```

```
#10    A = 1011;B = 1011;Bin = 0;
```

```
#10    A = 1100;B = 1100;Bin = 1;
```

```
#10    A = 1101;B = 1101;Bin = 0;
```

```
#10    A = 1110;B = 1110;Bin = 1;
```

```
#10    A = 1111;B = 1111;Bin = 0;
```

```
// Add stimulus here
```

```
end
```

```
endmodule
```

Simulations :

