

University of Engineering and Technology, Taxila

Department of Computer Engineering



Lab Report 02

For the Course of DSD lab

Submitted By: Muhammad Ibrahim (21-CP-26)

Section: Omega

Lab Instructor: Sir Shahid Ali

Course Instructor: Dr. Abdul rehman aslam

Date: 20-01-24.

Course Title: DSD Lab

Lab Tasks

Questions:

1. Design and Simulate four-input OR, XOR and XNOR gates using 2 input primitive gates

Code:

```
module q1(  
    input wire a, b, c, d,  
    output wire or_out, xor_out, xnor_out  
);  
  
    wire ab_or, cd_or;  
    wire ab_xor, cd_xor;  
    wire xnor_temp;  
  
    assign ab_or = a | b;  
    assign cd_or = c | d;  
  
    assign ab_xor = a ^ b;  
    assign cd_xor = c ^ d;  
  
    assign xnor_temp = ~(ab_xor | cd_xor);  
  
    assign or_out = ab_or | cd_or;  
  
    assign xor_out = ab_xor ^ cd_xor;  
    assign xnor_out = xnor_temp;  
endmodule
```

timescale 1ns / 1ps

//

// Company:

// Engineer:

//

// Create Date: 12:45:09 01/17/2024

// Design Name:

// Module Name: q1

// Project Name:

// Target Devices:

// Tool versions:

```
// Description:
```

```
//
```

```
// Dependencies:
```

```
//
```

```
// Revision:
```

```
// Revision 0.01 - File Created
```

```
// Additional Comments:
```

```
//
```

```
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
```

```
module q1(
```

```
    input wire a, b, c, d,
```

```
    output wire or_out, xor_out, xnor_out
```

```
);
```

```
    wire ab_or, cd_or;
```

```
    wire ab_xor, cd_xor;
```

```
    wire xnor_temp;
```

```
    assign ab_or = a | b;
```

```
    assign cd_or = c | d;
```

```
    assign ab_xor = a ^ b;
```

```
    assign cd_xor = c ^ d;
```

```
    assign xnor_temp = ~(ab_xor | cd_xor);
```

```
    assign or_out = ab_or | cd_or;
```

```
    assign xor_out = ab_xor ^ cd_xor;
```

```
    assign xnor_out = xnor_temp;
```

```
endmodule
```

TestBench:

```
// Create Date: 13:00:06 01/17/2024
```

```
// Design Name: q1
```

```
// Module Name: C:/Users/Ibrahim/Desktop/New folder/CP21_26_Lab2_Qn1/q1test.v
```

```
// Project Name: CP21_26_Lab2_Qn1
```

```
module q1test;
```

```
    // Inputs
```

```
    reg a;
```

```
    reg b;
```

```
    reg c;
```

```
    reg d;
```

```
    // Outputs
```

```
    wire or_out;
```

```
    wire xor_out;
```

```
    wire xnor_out;
```

```
    // Instantiate the Unit Under Test (UUT)
```

```
    q1 uut (
```

```
        .a(a),
```

```
        .b(b),
```

```
        .c(c),
```

```
        .d(d),
```

```
        .or_out(or_out),
```

```
        .xor_out(xor_out),
```

```
        .xnor_out(xnor_out)
```

```
    );
```

```
    initial begin
```

```
        // Initialize Inputs
```

```
        a = 0;
```

```
b = 0;
```

```
c = 0;
```

```
d = 0;
```

```
// Wait 100 ns for global reset to finish
```

```
#100;
```

```
// Test sequence
```

```
// Case 1: a=0, b=0, c=0, d=0
```

```
#10 a = 0; b = 0; c = 0; d = 0;
```

```
// Case 2: a=1, b=0, c=1, d=0
```

```
#10 a = 1; b = 0; c = 1; d = 0;
```

```
// Case 3: a=1, b=1, c=0, d=1
```

```
#10 a = 1; b = 1; c = 0; d = 1;
```


```
// Add more test cases as needed
```

```
end
```

```
endmodule
```

```
module qltest;
  // Inputs
  reg a;
  reg b;
  reg c;
  reg d;
  // Outputs
  wire or_out;
  wire xor_out;
  wire xnor_out;
  // Instantiate the Unit Under Test (UUT)
  ql uut (
    .a(a),
    .b(b),
    .c(c),
    .d(d),
    .or_out(or_out),
    .xor_out(xor_out),
    .xnor_out(xnor_out)
  );
  initial begin
    a = 0;
    b = 0;
    c = 0;
    d = 0;
    #100;
    // Test sequence
    #10 a = 0; b = 0; c = 0; d = 0;
    #10 a = 1; b = 0; c = 1; d = 0;
    #10 a = 1; b = 1; c = 0; d = 1;
  end
endmodule
```

Simulations :

 

		125,743 ps						
Name	Value	125,740 ps	125,742 ps	125,744 ps	125,746 ps	125,748 ps	125,750 ps	125,752 ps
or_out	1							
xor_out	0							
xnor_out	0							
a	1							
b	0							
c	1							
d	0							

X1: 125,743 ps

Task 2:

- Simulate the design given in Figure. 1 using gate level modeling.

 


Figure 1: Design-1 for Lab Tasks

Code:

```

`timescale 1ns / 1ps

////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////

// Company:

// Engineer:

//

// Create Date: 13:20:54 01/17/2024

// Design Name:

// Module Name: q2

// Project Name:
  
```

```

// Target Devices:

// Tool versions:

// Description:

//

// Dependencies:

//

// Revision:

// Revision 0.01 - File Created

// Additional Comments:

//

/////////////////////////////////////////////////////////////////

module q2(input wire a, b, c, d,

    output wire y_xor);

wire w1;

wire w2;

and a1 (w1,a,b);

or a2 (w2,c,d);

xor a3 (y_xor,w1,w2);

endmodule

module q2(input wire a, b, c, d,
    output wire y_xor);

wire w1;
wire w2;
and a1 (w1,a,b);
or a2 (w2,c,d);
xor a3 (y_xor,w1,w2);

endmodule

```

TestBench:

`timescale 1ns / 1ps

//

// Company:

// Engineer:

//

// Create Date: 14:46:09 01/17/2024

// Design Name: q2

// Module Name: C:/Users/Ibrahim/Desktop/New folder/CP21_26_Lab1_Qn2/q2test.v

// Project Name: CP21_26_Lab1_Qn2

// Target Device:

// Tool versions:

// Description:

//

// Verilog Test Fixture created by ISE for module: q2

//

// Dependencies:

//

// Revision:

// Revision 0.01 - File Created

// Additional Comments:

//

//

module q2test;

 // Inputs

 reg a;

 reg b;

 reg c;

 reg d;

 // Outputs

 wire y_xor;

```
q2 uut(  
    .a(a),  
    .b(b),  
    .c(c),  
    .d(d),  
    .y_xor(y_xor)  
);
```

```
initial begin
```

```
// Test sequence
```

```
// Case 1: a=0, b=0, c=0, d=0
```

```
#10 a = 0; b = 0; c = 0; d = 0;
```

```
// Case 2: a=1, b=0, c=1, d=0
```

```
#10 a = 1; b = 0; c = 1; d = 0;
```

```
// Case 3: a=1, b=1, c=0, d=1
```

```
#10 a = 1; b = 1; c = 0; d = 1;
```



```
// Wait 100 ns for global reset to finish
```

```
#100;
```

```
// Add stimulus here
```

```
end
```

```
endmodule
```

  Task 3:

Simulate the gate level model of 4 to 1 Mux using Verilog (HDL).

 


Figure 2: 4 x 1 Multiplexer

Code:

```

module q3 (
  input A,B,C,D,[1:0]S,
  output y
);
wire w1,w2,w3,w4,n1,n2;
not x3(n1,S[0]);
not x2(n2,S[1]);
and a1(w1,A,n1,n2);
and a2(w2,B,S[0],n2);
and a3(w3,C,n1,S[1]);
and a4(w4,D,S[0],S[1]);
or o1(y,w1,w2,w3,w4);

endmodule

```

```

module q3 (
    input A,B,C,D, [1:0]S,
    output y
);
wire w1,w2,w3,w4,n1,n2;
not x3(n1,S[0]);
not x2(n2,S[1]);
and a1(w1,A,n1,n2);
and a2(w2,B,S[0],n2);
and a3(w3,C,n1,S[1]);
and a4(w4,D,S[0],S[1]);
or o1(y,w1,w2,w3,w4);
endmodule

```

TestBench:

```
`timescale 1ns / 1ps
```

```
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
```

```
// Company:
```

```
// Engineer:
```

```
//
```

```
// Create Date: 17:02:11 01/17/2024
```

```
// Design Name: q3
```

```
// Module Name: C:/Users/Ibrahim/Desktop/New folder/CP21_26_Lab2_q3/Q3test.v
```

```
// Project Name: CP21_26_Lab2_q3
```

```
// Target Device:
```

```
// Tool versions:
```

```
// Description:
```

```
//
```

```
// Verilog Test Fixture created by ISE for module: q3
```

```
//
```

```
// Dependencies:
```

```
//
```

```
// Revision:
```

```
// Revision 0.01 - File Created
```

```
// Additional Comments:
```

```
//
```

```
////////////////////////////////////////////////////////////////
```

```
module Q3test;
```

```
    // Inputs
```

```
    reg A, B, C, D;
```

```
    reg [1:0] S;
```

```
    // Output
```

```
    wire y;
```

```
    // Instantiate the module
```

```
    q3 uut (
```

```
        .A(A),
```

```
        .B(B),
```

```
        .C(C),
```

```
        .D(D),
```

```
        .S(S),
```

```
        .y(y)
```

```
    );
```

```
initial begin
```

```
    // Initialize inputs
```

```
    A = 0;
```

```
    B = 1;
```

```
    C = 0;
```

```
    D = 1;
```

```
    S = 2'b00;
```

```
    #10 A = 1;
```

```
    #10 B = 0;
```

```
    #10 C = 1;
```

```
    #10 D = 0;
```

```
    #10 S = 2'b01;
```

```
end
```

```
endmodule
```

```

module Q3test;
    // Inputs
    reg A, B, C, D;
    reg [1:0] S;
    // Output
    wire y;
    // Instantiate the module
    q3 uut (
        .A(A),
        .B(B),
        .C(C),
        .D(D),
        .S(S),
        .y(y)
    );
initial begin
    // Initialize inputs
    A = 0;
    B = 1;
    C = 0;
    D = 1;
    S = 2'b00;
    #10 A = 1;
    #10 B = 0;
    #10 C = 1;
    #10 D = 0;
    #10 S = 2'b01;
end
endmodule

```

Simulations :

